

LED Circuit on a Breadboard

AIM


A simple LED circuit constructed on a breadboard using an LED, resistor, connecting wires, and a 9V battery.


Required Materials

- Breadboard
- LED
- Resistor
- Connecting wires
- 9V battery
- Battery connector

Procedure

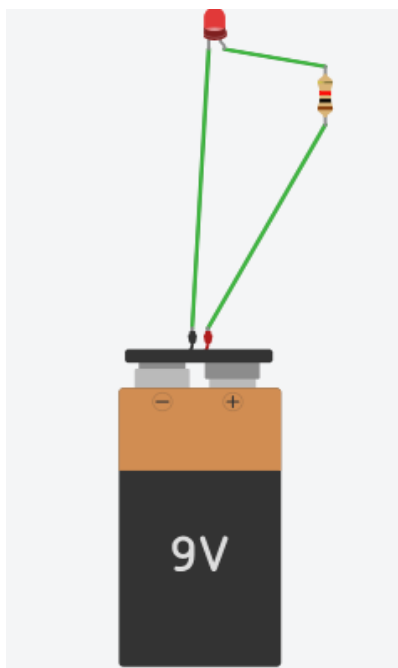1. Select the required components.
2. Place the LED on the breadboard.
3. Connect the resistor in series with the LED.
4. Connect the jumper wires to the appropriate breadboard terminals.
5. Connect the positive and negative terminals of the battery.
6. Switch on the power supply.
7. Check that the LED glows properly.



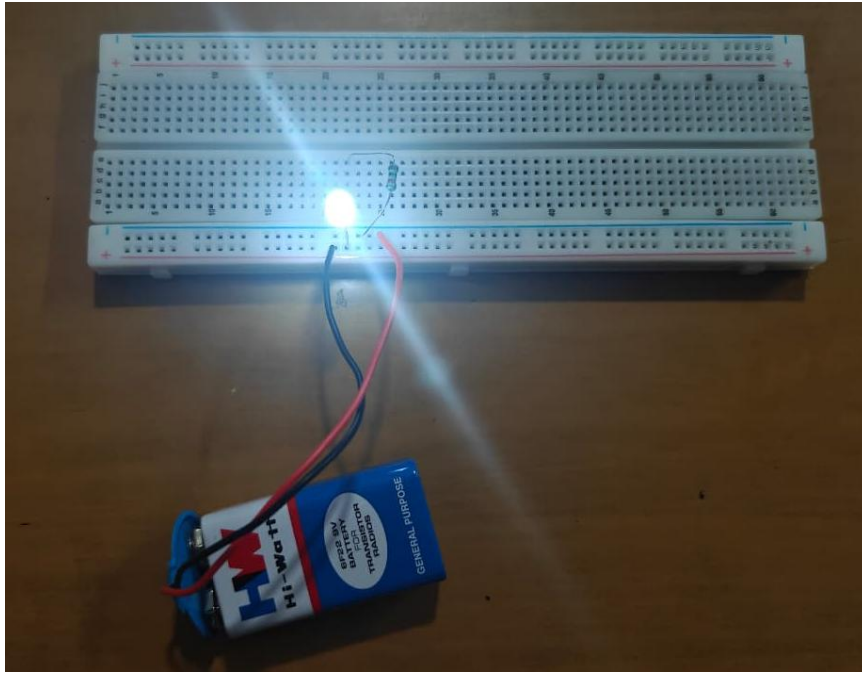

Notes

- Connect the LED with the correct polarity.
- Use a suitable resistor to protect the LED.
- Ensure all connections are tight and secure.
- Avoid short-circuiting the battery.
- Check the circuit carefully before connecting the power supply.